

◆ What is a Flip-Flop?

- A flip-flop is a small memory element in digital electronics.
  - It can store 1 bit of data: either 0 (LOW) or 1 (HIGH).
  - It is used in registers, counters, and memory circuits.
- 

### D Flip-Flop Description

A D flip-flop (Data or Delay flip-flop) is a sequential logic circuit that captures the value of the D (data) input at a particular clock edge (either rising or falling).

After the clock edge, the captured value is stored and appears at the output Q until the next active clock edge arrives.

It is widely used as a data storage element in digital systems such as registers, counters, and memory devices.

---

### Inputs and Outputs

- Inputs:
    - D (Data input)
    - Clock (CLK) – edge-triggered (rising ↑ or falling ↓)
    - *(Sometimes asynchronous inputs like Preset and Clear are also provided in practical ICs)*
  - Outputs:
    - Q (main output)
    - Q' (complement output)
- 

### Working Principle

The D flip-flop simply transfers the input D to output Q on every active clock edge.

- When the clock edge occurs (↑ or ↓ depending on design):
  - If  $D = 1 \rightarrow Q$  becomes 1 (Set)

- If  $D = 0 \rightarrow Q$  becomes 0 (Reset)

Between clock edges,  $Q$  remains constant, even if  $D$  changes.

Hence, the D flip-flop is also called a data latch or data buffer, because it holds the value of  $D$  until the next clock edge.

### Truth Table (Edge-Triggered)

CLK Edge D Next State ( $Q^{n+1}$ )

$\uparrow / \downarrow$       0 0 (reset)

$\uparrow / \downarrow$       1 1 (set)

*( $\uparrow$  means rising-edge triggered,  $\downarrow$  means falling-edge triggered depending on the flip-flop design)*

### Characteristic Equation

$$Q_{next} = D$$

This means the next state of the flip-flop is simply the value of  $D$  input at the clock edge.

### Implementation

- The D flip-flop can be constructed from an SR flip-flop by connecting:

$$S = D, R = \bar{D}$$

This eliminates the invalid state ( $S = R = 1$ ) problem of the SR flip-flop.

- Modern D flip-flops are edge-triggered and often built using master-slave latch configurations.

#### ◆ 1.1) Design Code

```
// D Flip-Flop
module d_ff (
    input wire D, CLK,
    output reg Q,
    output wire Qbar
);

    assign Qbar = ~Q;

    always @(posedge CLK) begin
        Q <= D;    // Q follows D only on posedge
    end
endmodule
```

◆ 1.2) Test Bench Code

```
module tb_d_ff;
    reg D, CLK;
    wire Q, Qbar;


    d_ff uut (.D(D), .CLK(CLK), .Q(Q), .Qbar(Qbar));

    // Clock
    initial begin
        CLK = 0;
        forever #5 CLK = ~CLK;
    end


    initial begin
        $monitor("T=%0t | CLK=%b D=%b | Q=%b Qbar=%b", $time, CLK, D, Q, Qbar);

        D=0; #10;
        D=1; #10;
        D=0; #10;
        D=1; #10;
        $finish;
    end
endmodule
```

### ◆ 1.3) Schematic

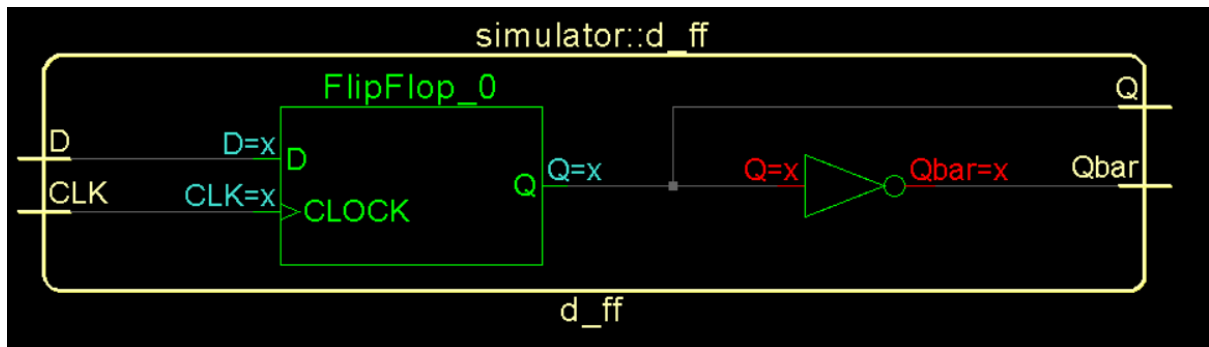

### ◆ 1.4) Wave Forms

 

## Applications

1. Data Storage:
  - Stores one bit of data per flip-flop — fundamental memory element.
2. Registers:
  - Multiple D flip-flops are combined to form shift registers and data registers.

3. Counters:

- Used in synchronous and asynchronous counters as intermediate storage.

4. Frequency Division:

- Can act as a simple frequency divider (divides input clock by 2 when connected with feedback).

5. Synchronization:

- Used to synchronize asynchronous signals with the system clock in digital systems (avoids metastability).

6. Finite State Machines (FSM):

- Used to store and update the present state of FSMs.