

◆ What is a Latch?

A latch is the simplest form of a memory element in digital electronics.

- It can store 1 bit of data.
 - It is level-sensitive → works as long as the Enable (or Clock) input is active.
 - Unlike flip-flops (which are edge-triggered), latches are transparent when enabled.
-

◆ D Latch

The D latch is also called a Data latch or Transparent latch.

👉 It is designed to overcome the invalid state problem of the SR latch.

How?

- In SR latch, when $S=1$ and $R=1$, it was invalid.
- The D latch removes this problem by having only one input (D).
- Internally, D latch ensures that $R = \text{NOT}(D)$ and $S = D$.

So you only give one input (D), and the latch stores it safely.

◆ Inputs and Outputs

- Inputs:
 - D (Data input)
 - Enable (or Clock/Control input, often called G or EN)
 - Outputs:
 - Q (main output)
 - \bar{Q} (complement output)
-

◆ Working (Truth Table)

When Enable = 1 (latch is open/transparent):

Enable D Q(next) Description

0 X Q(prev) Hold (no change, latch is closed)

1 0 0 Reset (Q = 0)

1 1 1 Set (Q = 1)

👉 When Enable = 1 → Q follows D ("transparent mode").

👉 When Enable = 0 → Q holds its last value ("latched mode").

◆ Symbol of D Latch

- Inputs: D, Enable
- Outputs: Q, \bar{Q}
- Often drawn as a block with D and EN on the left, Q/ \bar{Q} on the right.

◆ Why is it called "Transparent Latch"?

Because:

- When Enable = 1, the output Q is directly equal to input D → it looks "transparent".
- When Enable = 0, the latch becomes opaque and holds the last value.

◆ 1.1) Design Code

```
module d_latch (  
    input wire D,        // Data input  
    input wire EN,       // Enable input  
    output reg Q,        // Output  
    output wire Qbar     // Complement of Q  
);  
  
    assign Qbar = ~Q;  
  
    always @(*) begin  
        if (EN)          // If enable is high  
            Q <= D;      // Follow input  
        else  
            Q <= Q;      // Hold previous state  
        end  
    endmodule
```

◆ 1.2) Test Bench Code

```

module tb_d_latch;
    reg D, EN;
    wire Q, Qbar;


    d_latch uut (.D(D), .EN(EN), .Q(Q), .Qbar(Qbar));

    initial begin
        $monitor("Time=%0t | EN=%b D=%b | Q=%b Qbar=%b", $time, EN, D, Q, Qbar);


        // Initial state
        EN = 0; D = 0; #10;
        EN = 1; D = 1; #10; // Transparent, Q = D
        EN = 0; D = 0; #10; // Hold previous state
        EN = 1; D = 0; #10; // Transparent, Q = D
        EN = 0; D = 1; #10; // Hold previous state
        $finish;
    end
endmodule

```

◆ 1.3) Schematic

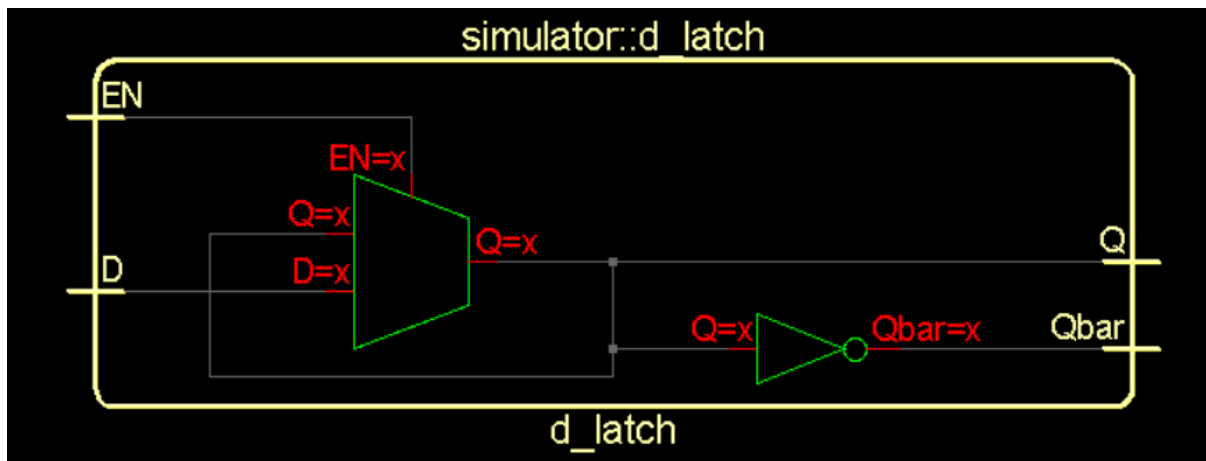

◆ 1.4) Wave Forms

 

◆ Applications

- Temporary data storage (1-bit memory).
- Level-sensitive registers.
- Used inside flip-flop construction (e.g., a D flip-flop is built using 2 D latches).
- Delay elements in sequential circuits.

